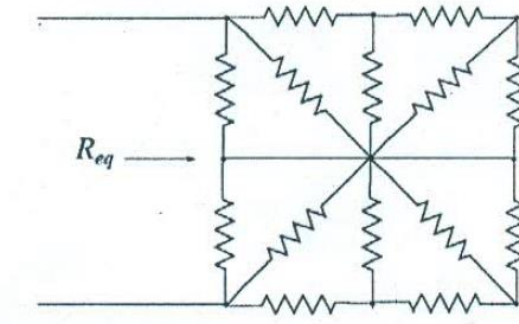


Term Test – 1

Marks – 20      Time – 60 Minutes      April 2017

1. Find equivalent resistance  $R_{eq}$  in the circuit below considering each of the resistor is  $20 \Omega$ .



2. Solve the following circuit using Nodal, Mesh and Superposition to find current through the connected ammeter. Compare all 3 results.

